




SN – 452

18

I Semester B.C.A. Degree Examination, November/December 2014
(Y2K8 Scheme)

(F + R)

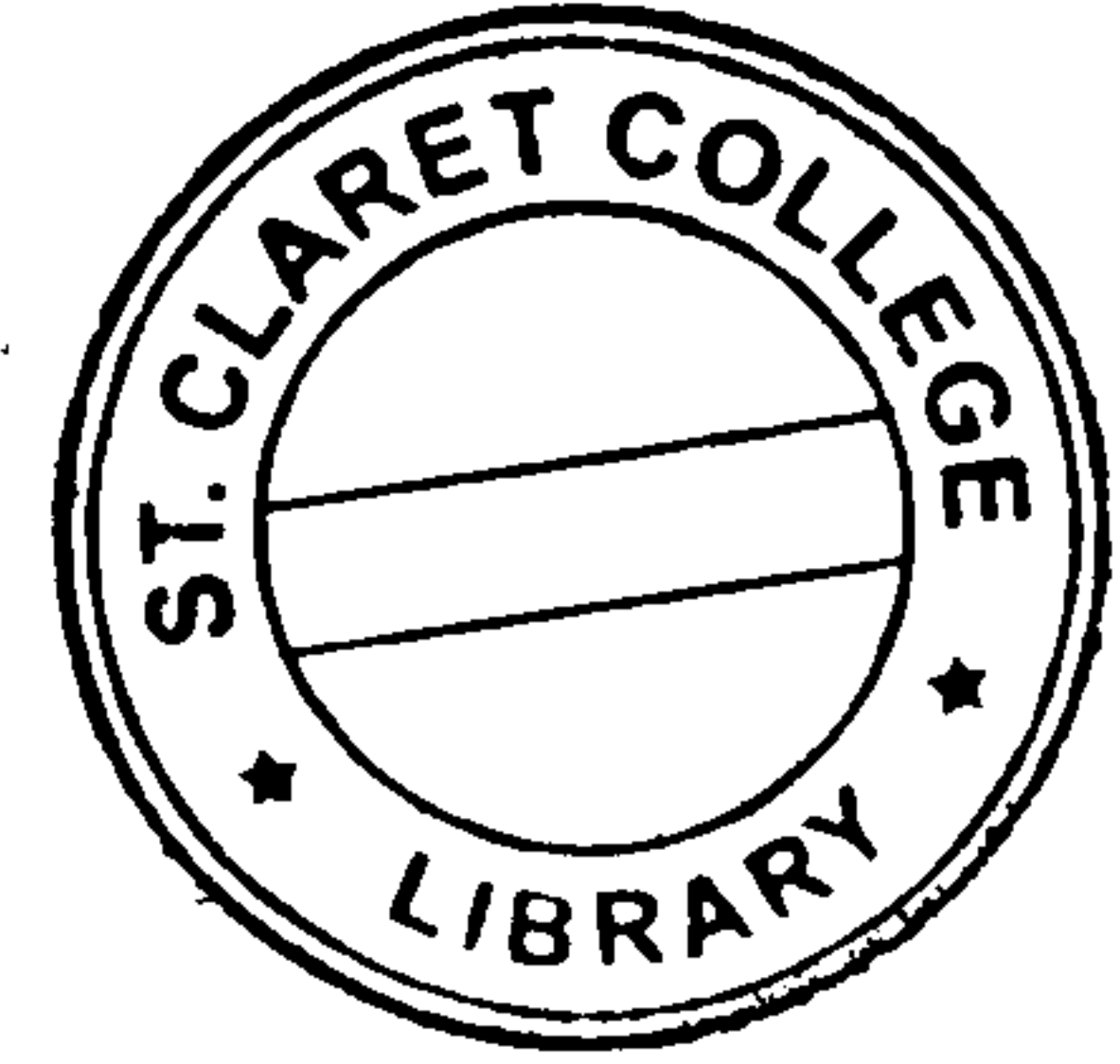COMPUTER SCIENCE
BCA 104 : Digital Electronics
(70 – 2011-12 & Onwards)
(60 – Prior to 2011-12)



Time : 3 Hours

Max. Marks : 60/70

Instruction : Section D should be answered by 2011-12 batch and Onwards.

SECTION – A

I. Answer **any ten each** carries **one** mark :

(10×1=10)

- 1) What is electric charge ?
- 2) Define KVL.
- 3) Write different energy bands.
- 4) Mention advantages of AC over DC.
- 5) What is doping ?
- 6) Write excess-3 code for $1100_{(2)}$.
- 7) Write any two boolean postulates.
- 8) What are universal gates ?
- 9) Expand POS and SOP.
- 10) Expand TTL.
- 11) What is parity bit ?
- 12) What is register ?

SECTION – B

II. Answer **any five** :

(5×3=15)

- 13) State and explain maximum power transfer theorem.
- 14) Explain the energy band theory of semiconductor.
- 15) What are the rules for binary arithmetic ?

P.T.O.



- 16) State and prove any three boolean postulates.
- 17) Explain n type and p type semiconductors.
- 18) Minimise the following standard SOP using K-Map

$$Y = A\bar{B}C + \bar{A}BC + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}\bar{C}.$$
- 19) Compare TTL with CMOS.
- 20) Explain the working of D Flip Flop with logic diagram and Truth table.

SECTION – C

- III. Answer **any five**, **each** carries **seven** marks. **(5×7=35)**
- 21) State and explain superposition theorem. 7
 - 22) Realise basic gates using universal gates with neat diagram. 7
 - 23) a) Simply using K-Map $F(A, B, C) = m(0, 2, 3, 5, 7)$. 4
 b) Explain XNOR gate. 3
 - 24) Explain BCA adder with neat circuit diagram and suitable example. 7
 - 25) Explain how to eliminate racing condition. 7
 - 26) Discuss the realisation of JK Flip Flop with timing diagram. 7
 - 27) What are registers ? Explain different types of shift registers. 7
 - 28) What are semiconductors ? Explain its different types. 7

SECTION – D

- IV. Answer **any one**. **Each** carries **ten** marks. **(1×10=10)**
- 29) a) Explain 8-bit decoder with diagram. 6
 b) What is error correction and error detection ? 4
 - 30) Write a short note on : **(2+4+4)**
 - a) Min. terms and max. terms
 - b) RS Flip Flop
 - c) 4-bit shift register.
-