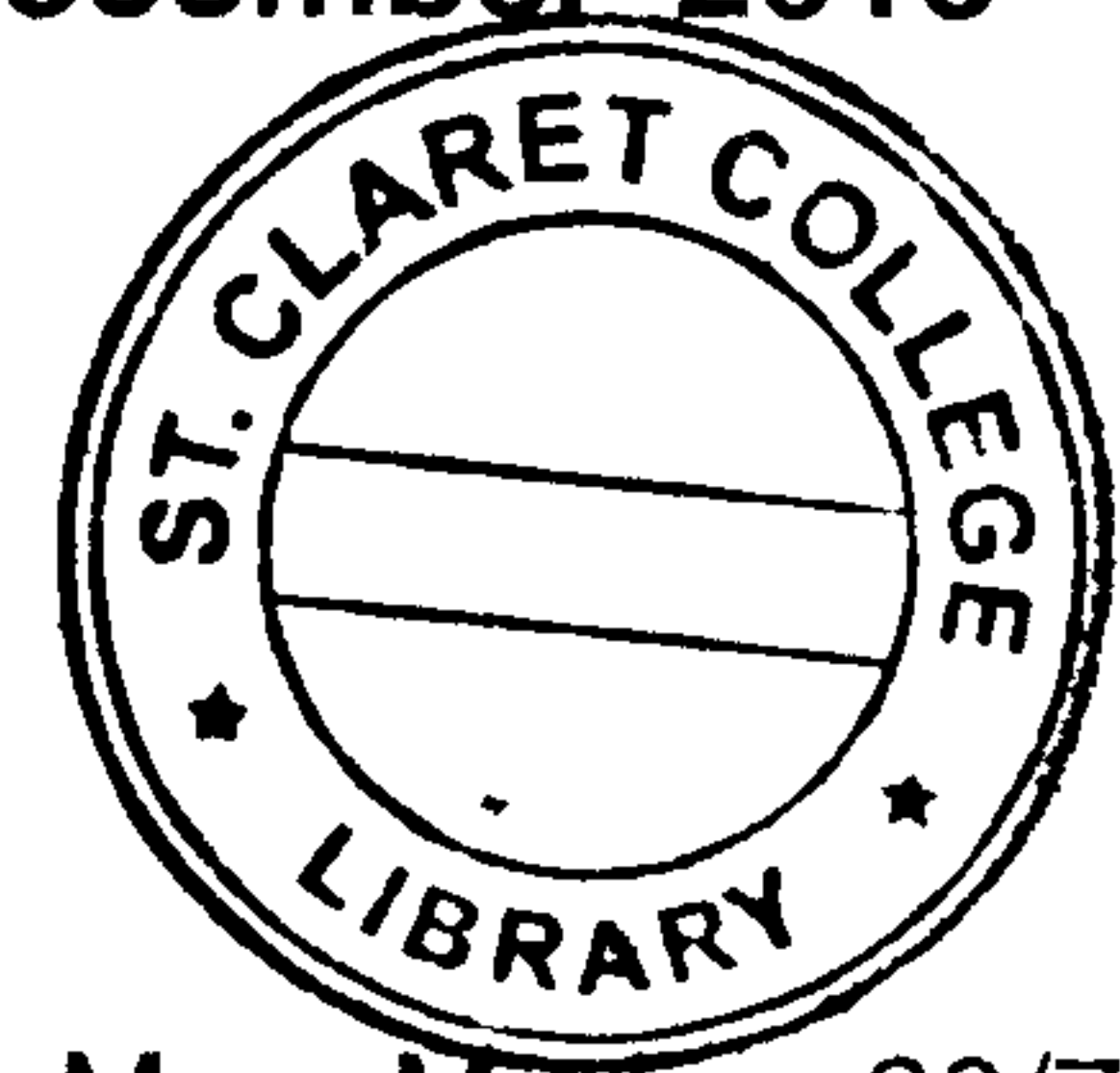




UN – 317

-14-

I Semester B.C.A. Degree Examination, November/December 2015  
(Repeaters) (Y2K8 Scheme)  
BCA 104 : ELECTRONICS  
70 – 2011-12 & Onwards  
60 – Prior to 2011-12



Time : 3 Hours

Max. Marks : 60/70

**Instruction** : Section D should be answered by 2011-12 batch Onwards.

SECTION – A

I. Answer **any ten, each** carries **one** mark.

(10×1=10)

- 1) State Kirchoff's voltage law.
- 2) Define Peak value of the wave.
- 3) Mention the types of energy bands.
- 4) What is semi conductor ?
- 5) Convert the decimal number 63 to binary.
- 6) Expand ASCII. What is its significance ?
- 7) Write any two postulates of Boolean algebra.
- 8) Write the symbol and truth table for AND gate.
- 9) Define minterm with example.
- 10) Define combinational logic circuit.
- 11) What is flip-flop ?
- 12) What is register ?

SECTION – B

II. Answer **any five, each** carries **3** marks.

(5×3=15)

- 13) State Ohm's law. Calculate the current following across 3 ohms resistor with a voltage of 18V.
- 14) Explain semiconductor using band theory.

P.T.O.



- 15) List any three properties of semiconductor.
- 16) Compare TTL & CMOS IC's.
- 17) Subtract 45 from 96 using 2's compliment method.
- 18) Explain half adder circuit with truth table.
- 19) Explain the working of T-flip flop with logic diagram.
- 20) Explain the applications of Shift register.

## SECTION – C

III. Answer **any five**, **each** carries **7** marks.

(5×7=35)

- 21) Explain the forward and reverse bias of PN diode.
- 22) State and explain Thevenin's theorem.
- 23) Realize the basic gates using Universal gates.
- 24) a) State and prove De Morgan's theorem.  
b) Define SOP & POS.
- 25) Simplify using K-map.  
$$F(A,B,C,D) = \sum m(0, 2, 3, 5, 7, 11, 13) + d(1, 7, 10) .$$
- 26) Explain 4-bit adder-subtractor circuit with neat diagram and truth table.
- 27) Discuss the realization of JK flip-flop with a neat diagram.
- 28) Explain the different types of shift registers.

## SECTION – D

(Only for 2011-12 and onwards)

IV. Answer **any one each** carries **10** marks.

(1×10=10)

- 29) a) Explain half wave rectifier with a neat diagram. 5  
b) Explain parity generator and parity checker. 5
  - 30) a) Explain the working of full adder circuit with the logic diagram. 5  
b) What is RS flip-flop ? Explain clocked RS flip-flop. 5
-