



SS – 694

39

**V Semester B.C.A. Degree Examination, November/December 2018
(Y2K8) (Repeaters)
COMPUTER SCIENCE
BCA 502 : Computer Architecture**

Time : 3 Hours

Max. Marks : 90/100

Instructions : 1) **100 marks for students of 2011 – 12 onwards (including Section – D).**


2) **90 marks for students prior to 2011 – 12 (excluding Section – D)**

SECTION – A

I. Answer **any ten** questions :

(10×2=20)

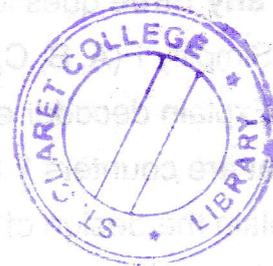- 1) What are universal gates ?
- 2) State DeMorgan's theorem.
- 3) Mention the different logic families of IC.
- 4) What is encoder ?
- 5) What is state table ?
- 6) Define Baud rate.
- 7) What is program status word ?
- 8) What do you mean by transfer rate ?
- 9) Convert $(41.6875)_{10}$ to binary.
- 10) What is primary memory ? Give examples.
- 11) What is polling ?
- 12) What is cache memory ?



SECTION – B

II. Answer **any five** questions :

(5×5=25)

- 13) Explain the working of JK Flip Flop.
- 14) What are combination circuit ? Draw the block diagram and write the truth table of half adder.

P.T.O.



- 15) What are multiplexer ? Explain 4 to 1 MUX.
- 16) Explain ROM with a neat block diagram and write a note on different types of ROM.
- 17) With example explain the steps of is complement subtraction.
- 18) Explain any five data transfer instruction.
- 19) What are interrupts ? Explain various types of interrupts.
- 20) Write short on isolated and memory mapped I/O.

SECTION - C

III. Answer **any three** questions :

(3×15=45)

- 21) a) Simplify $F(A, B, C, D) = \sum m(1, 3, 7, 11, 15) + \sum d(0, 2, 5)$ using K-map. **8**
- b) Explain decoder expansion with a neat diagram. **7**
- 22) What are counters ? Explain four bit counter in detail.
- 23) Explain the design of basic computer with flowchart.
- 24) a) What is asynchronous data transfer ? Explain source initiated strobe for data transfer. **8**
- b) Explain with example different types of instruction format. **7**
- 25) a) Explain the flowchart of interrupt cycle. **7**
- b) Differentiate between CISC and RISC instructions. **8**

SECTION - D

IV. Answer **any one** question :

(1×10=10)

- 26) What are sequential circuit ? Write the state table and draw the state diagram for input equations :

$$D_A = A'x + B'x$$

$$D_B = A'x$$

Output equation

$$Y = Ax + Bx$$

- 27) Explain the various addressing modes.
-