



**GN-445**

102668

10

I Semester B.C.A. Examination, December - 2019  
(CBCS) (F+R) 2014-15 and Onwards)

**COMPUTER SCIENCE**  
**BCA-104 T : Digital Electronics**

Time : 3 Hours

Max. Marks : 70


**Instruction :** Answer **all** sections.

**SECTION - A**

**I.** Answer **any ten** questions :

**10x2=20**

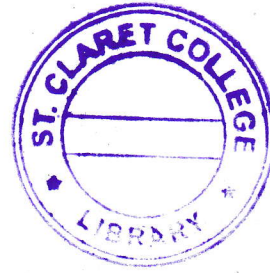1. State and explain Ohm's law.
2. What is Conductor ? Give examples.
3. Define PN diode. Explain forward bias.
4. Define Peak factor and Form factor.
5. What is NAND gate ? Write truth table and logic symbol for it.
6. Convert  $27.52_{(10)}$  to Octal and Hexa-decimal.
7. Find 2's complement of  $1110101_{(2)}$ .
8. Convert  $101101_{(2)}$  to gray code.
9. What is half-adder ? Write its logic circuit.
10. Define shift register. List its modes of operation.
11. What is Combinational Circuit ? Give examples.
12. If two resistors of  $5\Omega$  each are connected in parallel, what is the equivalent total resistance ?



**P.T.O.**




## SECTION - B

II. Answer **any five** of the following questions.

**5x10=50**

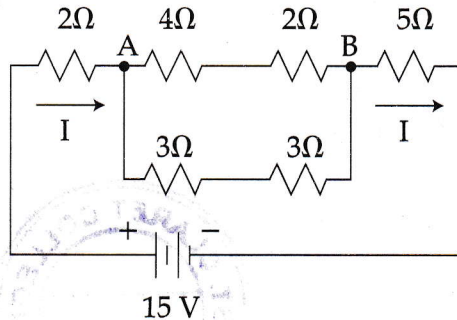13. (a) State and prove De-morgan's Law. **5**  
 (b) Realize basic gates using NOR gate. **5**
14. (a) Explain Thevenin's theorem in detail. **5**  
 (b) For the below resistive network, find the current through  $5\Omega$  resistor and voltage across node AB. **5**



15. (a) Explain full adder with truth table and logic circuit. **5**  
 (b) What is data selector? Explain the  $4 \times 1$  multiplexer. **5**
16. (a) What is rectifier? Explain Full-wave rectifier with a neat diagram. **5**  
 (b) Explain Kirchoff's voltage and current laws. **5**
17. (a) What is energy band? Explain all the three energy bands. **5**  
 (b) Differentiate between intrinsic and extrinsic semiconductors. **5**
18. (a) Simplify  $AB + A(\bar{B} + C) + B(\bar{B} + \bar{C})$  using boolean algebra and draw logic circuit for simplified equation. **5**  
 (b) Simplify SOP using 4-variable K-Map **5**  
 $F(ABCD) = \sum m(1, 5, 7, 8, 9, 13, 15) + \sum d(3, 12)$ .
19. (a) Explain JK flip-flop with a block diagram. Show how to convert a JK flip-flop to flip-flop. **5**  
 (b) What is shift register? Explain modes of operation of registers in brief. **5**
20. (a) Subtract  $228_{(10)} - 150_{(10)}$  using the 2's complement method. **5**  
 (b) Explain 4 bit parallel adder with a neat diagram. **5**